
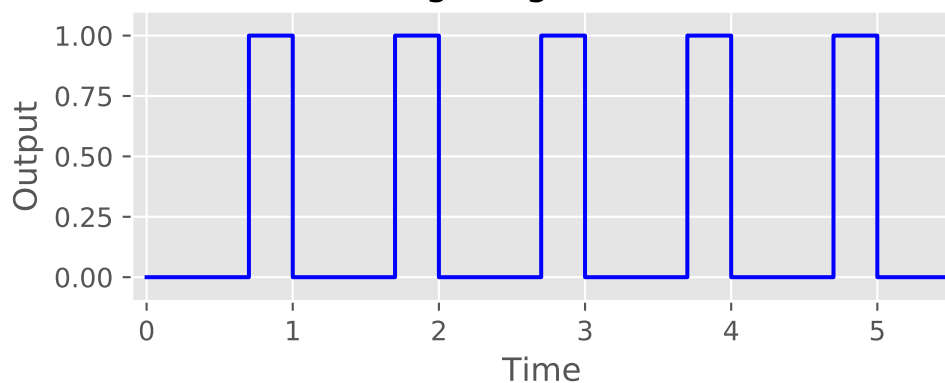



Timing Diagram for Clk

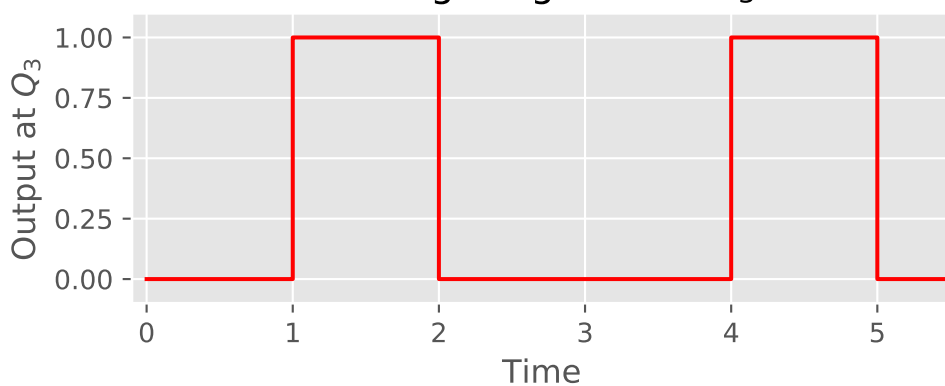

Timing Diagram for D_3



Timing Diagram for D_5

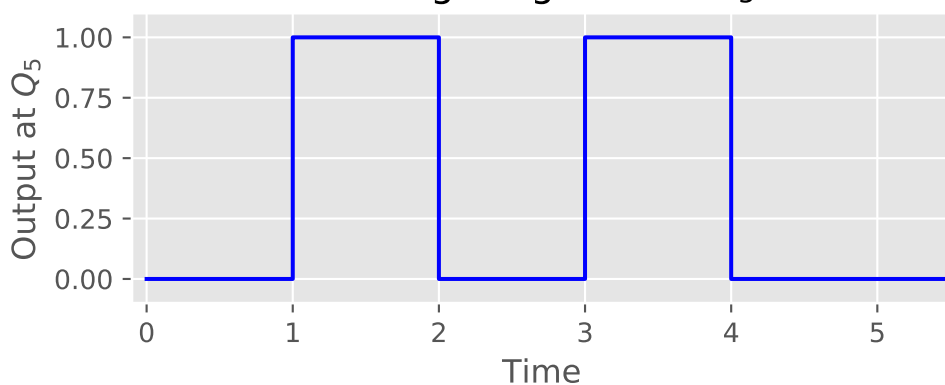

Timing Diagram for $Y = Q_3 + Q_5$

