

Digital Logic Design Assignment 9 - EC2018-31

Priyansh Agrahari

December 16, 2020

1 Question:

A four-variable Boolean function is realized using 4x1 multiplexers as shown in the figure:

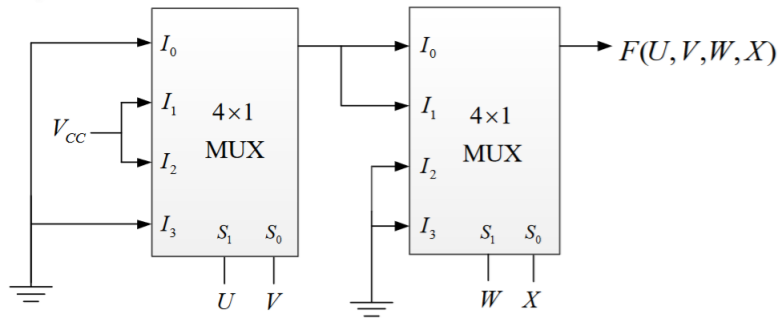


Figure 1: Question figure

The minimized expression for $F(U, V, W, X)$ is

- (A) $(U V + \overline{U} \overline{V}) \overline{W}$
- (B) $(U V + \overline{U} \overline{V}) (\overline{W} \overline{X} + \overline{W} X)$
- (C) $(U \overline{V} + \overline{U} V) \overline{W}$
- (D) $(U \overline{V} + \overline{U} V) (\overline{W} \overline{X} + \overline{W} X)$

2 Solution:

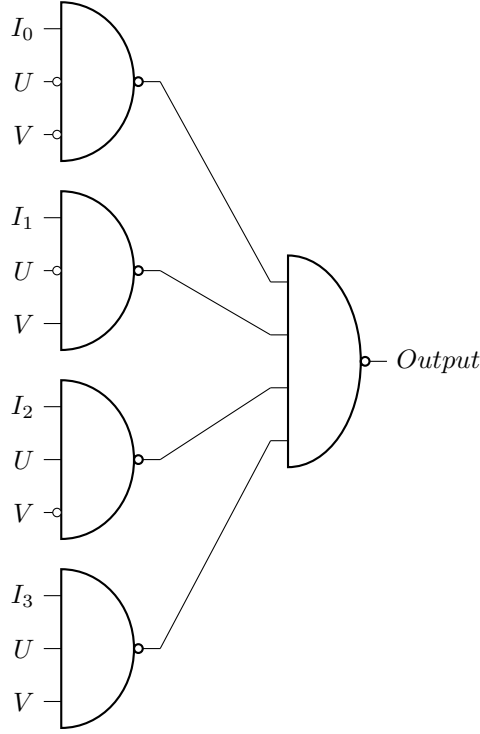


Figure 2: *Logic circuit equivalent of 4x1 MUX used to solve this problem*

Since we have I_0 and I_3 grounded, we can take their boolean equivalents to be 0. Then, we get the following equation:

$$Output = \overline{(U + \bar{V})}(\bar{U} + V) \quad (1)$$

which can be further simplified (using de Morgan's law) to obtain:

$$Output = U\bar{V} + \bar{U}V \quad (2)$$

Moving further, the same logic can be used to obtain the result of the second MUX. Since in this case, I_2 and I_3 are grounded; hence by taking their boolean equivalents to be 0, we get the following equation from the second MUX:

$$F = \overline{\overline{(Output.\bar{W}.\bar{X})}.\overline{(Output.\bar{W}.X)}} \quad (3)$$

simplifying, we get:

$$F = Output.\bar{W}.\bar{X} + Output.\bar{W}.X \quad (4)$$

after placing the value of *Output* from eq.(2), and performing a few more manipulations, we get:

$$F = (U\bar{V} + \bar{U}V)\bar{W}(X + \bar{X}) \quad (5)$$

Since $X + \bar{X} = 1$, we finally get the desired equation:

$$F = (U\bar{V} + \bar{U}V)\bar{W} \quad (6)$$

Hence, the answer the given question is (C).

3 Truth Table

| U | V | W | X | F | Term |
|-----|-----|-----|-----|-----|-----------------------------|
| 0 | 0 | 0 | 0 | 0 | - |
| 0 | 0 | 0 | 1 | 0 | - |
| 0 | 0 | 1 | 0 | 0 | - |
| 0 | 0 | 1 | 1 | 0 | - |
| 0 | 1 | 0 | 0 | 1 | $\bar{U} V \bar{W} \bar{X}$ |
| 0 | 1 | 0 | 1 | 1 | $\bar{U} V \bar{W} X$ |
| 0 | 1 | 1 | 0 | 0 | - |
| 0 | 1 | 1 | 1 | 0 | - |
| 1 | 0 | 0 | 0 | 1 | $U \bar{V} \bar{W} \bar{X}$ |
| 1 | 0 | 0 | 1 | 1 | $U \bar{V} \bar{W} X$ |
| 1 | 0 | 1 | 0 | 0 | - |
| 1 | 0 | 1 | 1 | 0 | - |
| 1 | 1 | 0 | 0 | 0 | - |
| 1 | 1 | 0 | 1 | 0 | - |
| 1 | 1 | 1 | 0 | 0 | - |
| 1 | 1 | 1 | 1 | 0 | - |

Table 1: Truth Table for eq.(6)

4 K-map for the function $F(U,V,W,X)$

| | | UV | | | |
|------|----|------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| WX | 00 | 0 | 1 | 0 | 1 |
| | 01 | 0 | 1 | 0 | 1 |
| | 11 | 0 | 0 | 0 | 0 |
| | 10 | 0 | 0 | 0 | 0 |

Figure 3: K-map for SOP expression

The expression obtained using the K-map is the same as the one obtained earlier in eq.(6). Alternatively, we can also make a K-map for obtaining the POS expression:

| | | UV | | | |
|------|----|------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| WX | 00 | 0 | 1 | 0 | 1 |
| | 01 | 0 | 1 | 0 | 1 |
| | 11 | 0 | 0 | 0 | 0 |
| | 10 | 0 | 0 | 0 | 0 |

Figure 4: K-map for POS expression

The POS expression hence obtained is:

$$F = (U + V)(\overline{U} + \overline{V})\overline{W} \quad (7)$$

5 C implementation to verify Table 1

5.1 C code:

```
1 #include <stdio.h>
2 int main(void)
3 {
4     unsigned char U = 0x00, V = 0x01, W = 0x00, X = 0x00;
5     unsigned char F, one = 0x01;
6
7     F = (~W) & ( (U & (~V)) | ((~U) & V) );
8     printf("Using SOP form: F = %x\n", (F & one));
9
10    F = (U | V) & ((~U) | (~V)) & (~W);
11    printf("Using POS form: F = %x\n", (F & one));
12 }
```

5.2 Output:

```
1 Using SOP form: F = 1
2 Using POS form: F = 1
```
